

**CS:APP Chapter 4**  
**Computer Architecture**  
**Sequential**  
**Implementation**

**Randal E. Bryant**

***Carnegie Mellon University***

<http://csapp.cs.cmu.edu>

# Y86 Instruction Set


Byte	0	1	2	3	4	5	
nop	0	0					
halt	1	0					
rrmovl rA, rB	2	0	rA	rB			
irmovl V, rB	3	0	8	rB	V		
rmmovl rA, D(rB)	4	0	rA	rB	D		
mrmovl D(rB), rA	5	0	rA	rB	D		
OPl rA, rB	6	fn	rA	rB			
jXX Dest	7	fn	Dest				
call Dest	8	0	Dest				
ret	9	0					
pushl rA	A	0	rA	8			
popl rA	B	0	rA	8			
							addl 6 0
							subl 6 1
							andl 6 2
							xorl 6 3
							jmp 7 0
							jle 7 1
							j1 7 2
							je 7 3
							jne 7 4
							jge 7 5
							jg 7 6

CS:APP

# Building Blocks

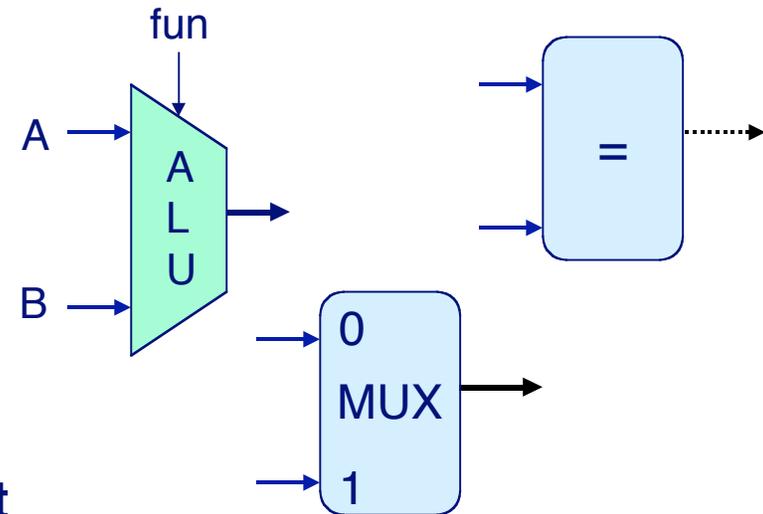
## Combinational Logic

- Compute Boolean functions of inputs
- Continuously respond to input changes
- Operate on data and implement control


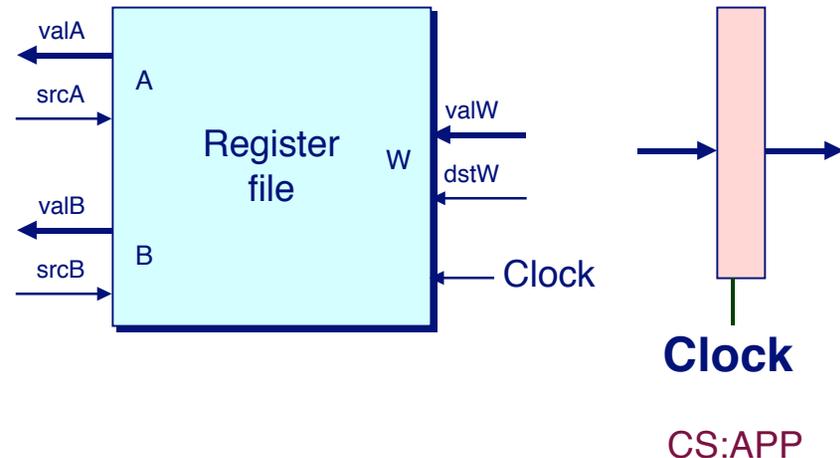
## Storage Elements

- Store bits
- Addressable memories
- Non-addressable registers
- Loaded only as clock rises



# Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
  - Parts we want to explore and modify

## Data Types

- `bool`: Boolean
  - `a, b, c, ...`
- `int`: words
  - `A, B, C, ...`
  - Does not specify word size---bytes, 32-bit words, ...

## Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

# HCL Operations

- Classify by type of value returned

## Boolean Expressions

- Logic Operations

- `a && b, a || b, !a`

- Word Comparisons

- `A == B, A != B, A < B, A <= B, A >= B, A > B`

- Set Membership

- `A in { B, C, D }`

» Same as `A == B || A == C || A == D`

## Word Expressions

- Case expressions

- `[ a : A; b : B; c : C ]`

- Evaluate test expressions `a, b, c, ...` in sequence

- Return word expression `A, B, C, ...` for first successful test


# SEQ Hardware Structure

## State

- Program counter register (PC)
- Condition code register (CC)
- Register File
- Memories
  - Access same memory space
  - Data: for reading/writing program data
  - Instruction: for reading instructions
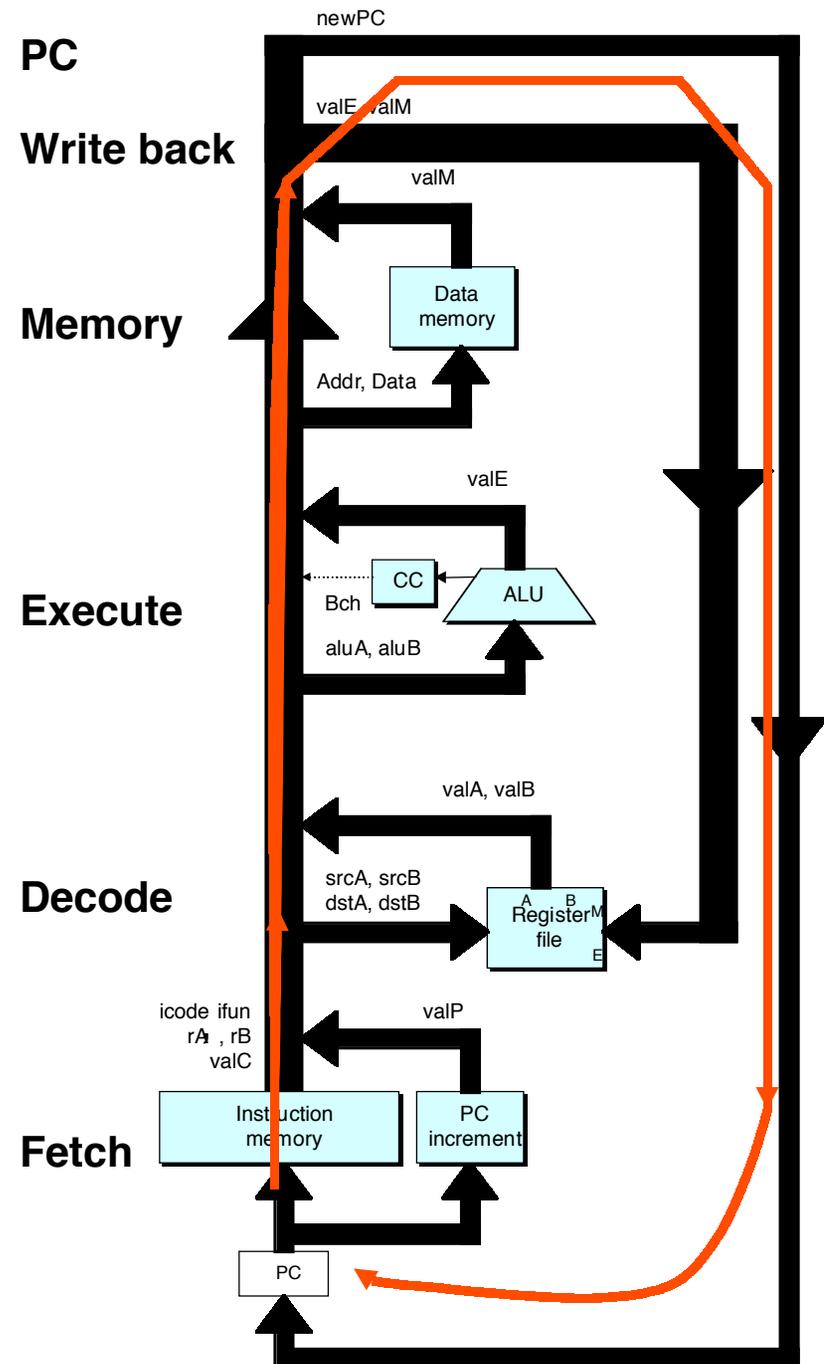
## Instruction Flow

- Read instruction at address specified by PC
- Process through stages
- Update program counter



# SEQ Stages

## Fetch

- Read instruction from instruction memory

## Decode

- Read program registers

## Execute

- Compute value or address

## Memory


- Read or write data

## Write Back


- Write program registers

## PC

- Update program counter

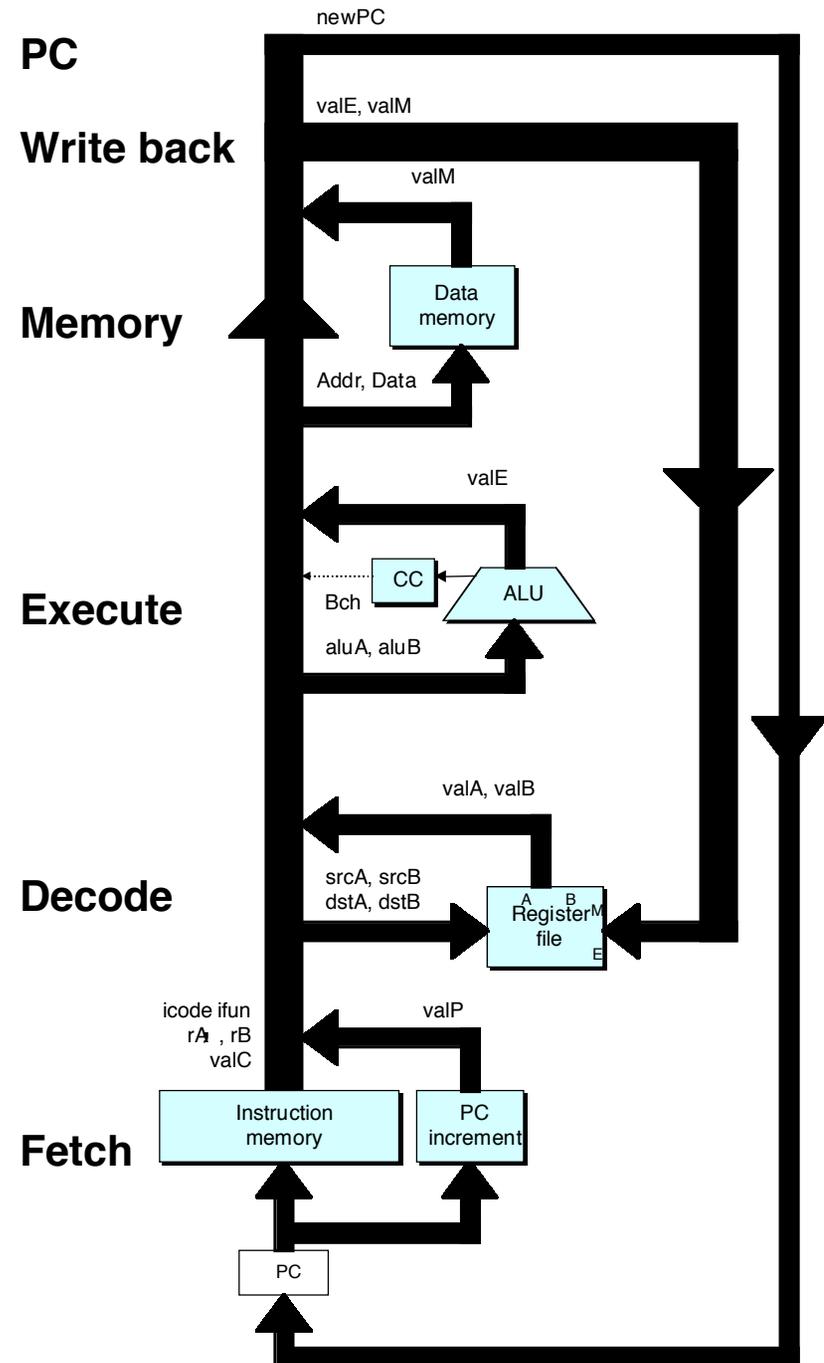

# Instruction Decoding

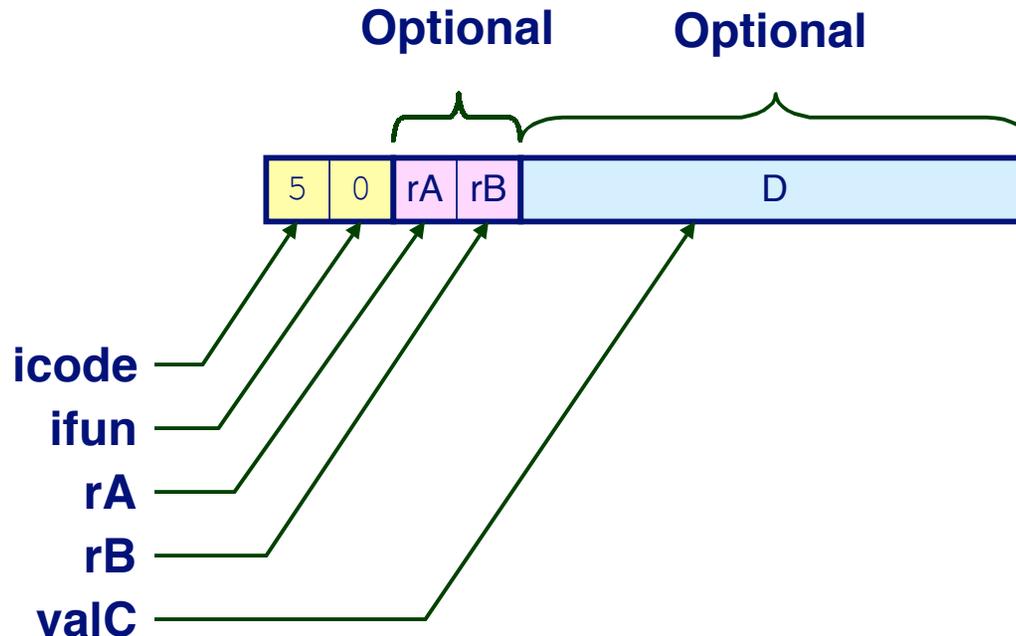

## Instruction Format

- Instruction byte      icode:ifun
- Optional register byte      rA:rB
- Optional constant word      valC

# Executing Arith./Logical Operation

OP1 rA, rB

6	fn	rA	rB
---	----	----	----

## Fetch

- Read 2 bytes

## Decode

- Read operand registers

## Execute

- Perform operation
- Set condition codes

## Memory

- Do nothing

## Write back

- Update register

## PC Update

- Increment PC by 2

# Stage Computation: Arith/Log. Ops

	OPI rA, rB	
Fetch	icode:ifun $\leftarrow$ M <sub>1</sub> [PC] rA:rB $\leftarrow$ M <sub>1</sub> [PC+1]	Read instruction byte Read register byte
	valP $\leftarrow$ PC+2	Compute next PC
Decode	valA $\leftarrow$ R[rA]	Read operand A
	valB $\leftarrow$ R[rB]	Read operand B
Execute	valE $\leftarrow$ valB OP valA	Perform ALU operation
	Set CC	Set condition code register
Memory		
Write back	R[rB] $\leftarrow$ valE	Write back result
	PC update	PC $\leftarrow$ valP

- Formulate instruction execution as sequence of simple steps
- Use same general form for all instructions

# Executing `rmmovl`

`rmmovl rA, D(rB)`

4	0	rA	rB	D	
---	---	----	----	---	--

## Fetch

- Read 6 bytes

## Decode

- Read operand registers

## Execute

- Compute effective address

## Memory

- Write to memory

## Write back

- Do nothing

## PC Update

- Increment PC by 6

# Stage Computation: `rmmovl`

	<code>rmmovl rA, D(rB)</code>	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$ $\text{rA:rB} \leftarrow M_1[\text{PC}+1]$ $\text{valC} \leftarrow M_4[\text{PC}+2]$ $\text{valP} \leftarrow \text{PC}+6$	Read instruction byte Read register byte Read displacement D Compute next PC
Decode	$\text{valA} \leftarrow R[\text{rA}]$ $\text{valB} \leftarrow R[\text{rB}]$	Read operand A Read operand B
Execute	$\text{valE} \leftarrow \text{valB} + \text{valC}$	Compute effective address
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
Write back		
PC update	$\text{PC} \leftarrow \text{valP}$	Update PC

- Use ALU for address computation

# Executing popl



## Fetch

- Read 2 bytes

## Decode

- Read stack pointer

## Execute

- Increment stack pointer by 4

## Memory

- Read from old stack pointer

## Write back

- Update stack pointer
- Write result to register

## PC Update


- Increment PC by 2

# Stage Computation: `popl rA`

	<code>popl rA</code>	
Fetch	<code>icode:ifun ← M<sub>1</sub>[PC]</code> <code>rA:rB ← M<sub>1</sub>[PC+1]</code>	Read instruction byte Read register byte
	<code>valP ← PC+2</code>	Compute next PC
Decode	<code>valA ← R[%esp]</code>	Read stack pointer
	<code>valB ← R [%esp]</code>	Read stack pointer
Execute	<code>valE ← valB + 4</code>	Increment stack pointer
Memory	<code>valM ← M<sub>4</sub>[valA]</code>	Read from stack
Write back	<code>R[%esp] ← valE</code>	Update stack pointer
	<code>R[rA] ← valM</code>	Write back result
PC update	<code>PC ← valP</code>	Update PC

- Use ALU to increment stack pointer
- Must update two registers
  - Popped value
  - New stack pointer

# Executing Jumps

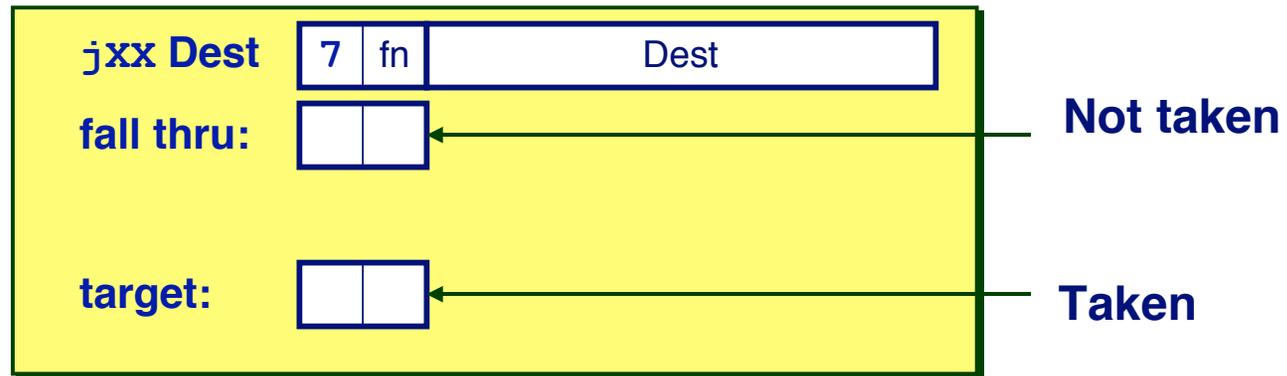

## Fetch

- Read 5 bytes
- Increment PC by 5

## Decode

- Do nothing

## Execute

- Determine whether to take branch based on jump condition and condition codes

## Memory

- Do nothing

## Write back

- Do nothing

## PC Update


- Set PC to Dest if branch taken or to incremented PC if not branch

# Stage Computation: Jumps

	jXX Dest	
Fetch	$icode:ifun \leftarrow M_1[PC]$	Read instruction byte
	$valC \leftarrow M_4[PC+1]$	Read destination address
	$valP \leftarrow PC+5$	Fall through address
Decode		
Execute	$Bch \leftarrow Cond(CC,ifun)$	Take branch?
Memory		
Write back		
PC update	$PC \leftarrow Bch ? valC : valP$	Update PC

- Compute both addresses
- Choose based on setting of condition codes and branch condition

# Executing call

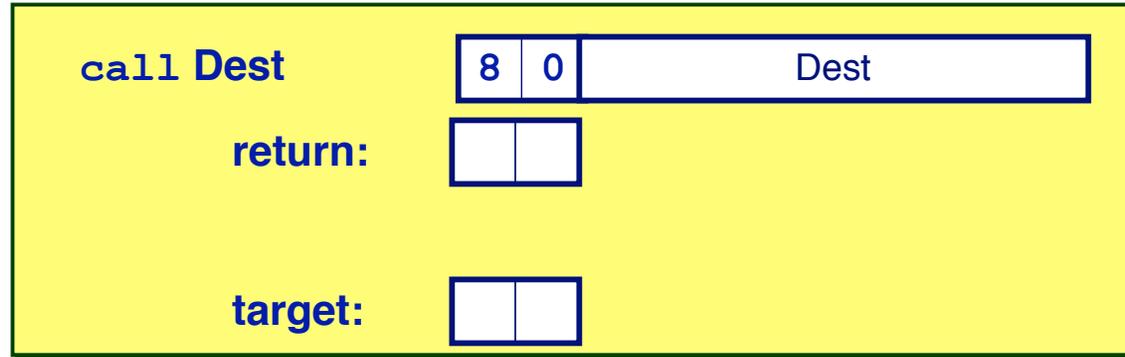

## Fetch

- Read 5 bytes
- Increment PC by 5

## Decode

- Read stack pointer

## Execute

- Decrement stack pointer by 4

## Memory

- Write incremented PC to new value of stack pointer

## Write back

- Update stack pointer

## PC Update


- Set PC to Dest

# Stage Computation: call

	call Dest	
Fetch	$icode:ifun \leftarrow M_1[PC]$	Read instruction byte
	$valC \leftarrow M_4[PC+1]$	Read destination address
	$valP \leftarrow PC+5$	Compute return point
Decode	$valB \leftarrow R[\%esp]$	Read stack pointer
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
Memory	$M_4[valE] \leftarrow valP$	Write return value on stack
Write back	$R[\%esp] \leftarrow valE$	Update stack pointer
PC update	$PC \leftarrow valC$	Set PC to destination

- Use ALU to decrement stack pointer
- Store incremented PC

# Executing `ret`

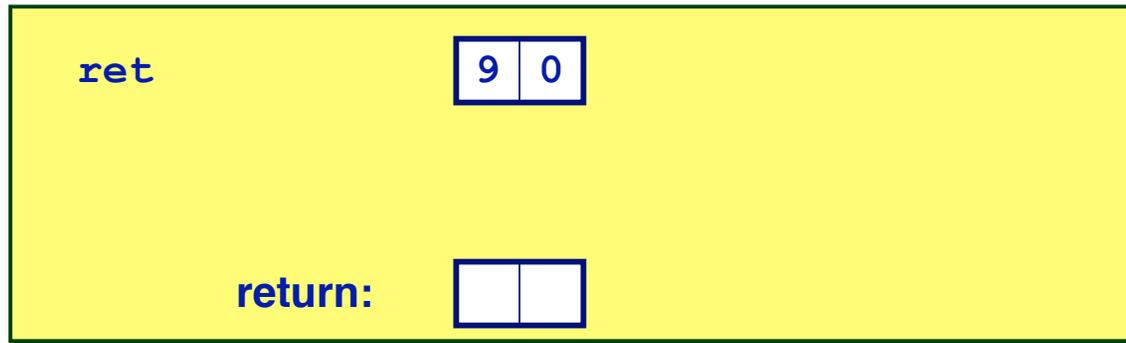

## Fetch

- Read 1 byte

## Decode

- Read stack pointer

## Execute

- Increment stack pointer by 4

## Memory

- Read return address from old stack pointer

## Write back

- Update stack pointer

## PC Update

- Set PC to return address

# Stage Computation: `ret`

		<code>ret</code>	
Fetch		<code>icode:ifun ← M<sub>1</sub>[PC]</code>	Read instruction byte
Decode		<code>valA ← R[%esp]</code> <code>valB ← R[%esp]</code>	Read operand stack pointer Read operand stack pointer
Execute		<code>valE ← valB + 4</code>	Increment stack pointer
Memory		<code>valM ← M<sub>4</sub>[valA]</code>	Read return address
Write back		<code>R[%esp] ← valE</code>	Update stack pointer
PC update		<code>PC ← valM</code>	Set PC to return address

- Use ALU to increment stack pointer
- Read return address from memory

# Computation Steps

		OPI rA, rB	
Fetch	icode,ifun	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
	rA,rB	$\text{rA:rB} \leftarrow M_1[\text{PC}+1]$	Read register byte
	valC		[Read constant word]
	valP	$\text{valP} \leftarrow \text{PC}+2$	Compute next PC
Decode	valA, srcA	$\text{valA} \leftarrow R[\text{rA}]$	Read operand A
	valB, srcB	$\text{valB} \leftarrow R[\text{rB}]$	Read operand B
Execute	valE	$\text{valE} \leftarrow \text{valB OP valA}$	Perform ALU operation
	Cond code	Set CC	Set condition code register
Memory	valM		[Memory read/write]
Write back	dstE	$R[\text{rB}] \leftarrow \text{valE}$	Write back ALU result
	dstM		[Write back memory result]
PC update	PC	$\text{PC} \leftarrow \text{valP}$	Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

# Computation Steps

		call Dest	
Fetch	icode,ifun	$icode:ifun \leftarrow M_1[PC]$ $valC \leftarrow M_4[PC+1]$ $valP \leftarrow PC+5$	Read instruction byte
	rA,rB		[Read register byte]
	valC		Read constant word
	valP		Compute next PC
Decode	valA, srcA	$valB \leftarrow R[\%esp]$	[Read operand A]
	valB, srcB		Read operand B
Execute	valE	$valE \leftarrow valB + -4$	Perform ALU operation
	Cond code		[Set condition code reg.]
Memory	valM	$M_4[valE] \leftarrow valP$	[Memory read/write]
Write back	dstE	$R[\%esp] \leftarrow valE$	[Write back ALU result]
	dstM		Write back memory result
PC update	PC	$PC \leftarrow valC$	Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

# Computed Values

## Fetch

<b>icode</b>	<b>Instruction code</b>
<b>ifun</b>	<b>Instruction function</b>
<b>rA</b>	<b>Instr. Register A</b>
<b>rB</b>	<b>Instr. Register B</b>
<b>valC</b>	<b>Instruction constant</b>
<b>valP</b>	<b>Incremented PC</b>

## Decode

<b>srcA</b>	<b>Register ID A</b>
<b>srcB</b>	<b>Register ID B</b>
<b>dstE</b>	<b>Destination Register E</b>
<b>dstM</b>	<b>Destination Register M</b>
<b>valA</b>	<b>Register value A</b>
<b>valB</b>	<b>Register value B</b>

## Execute

- **valE** **ALU result**
- **Bch** **Branch flag**


## Memory

- **valM** **Value from memory**


# SEQ Hardware
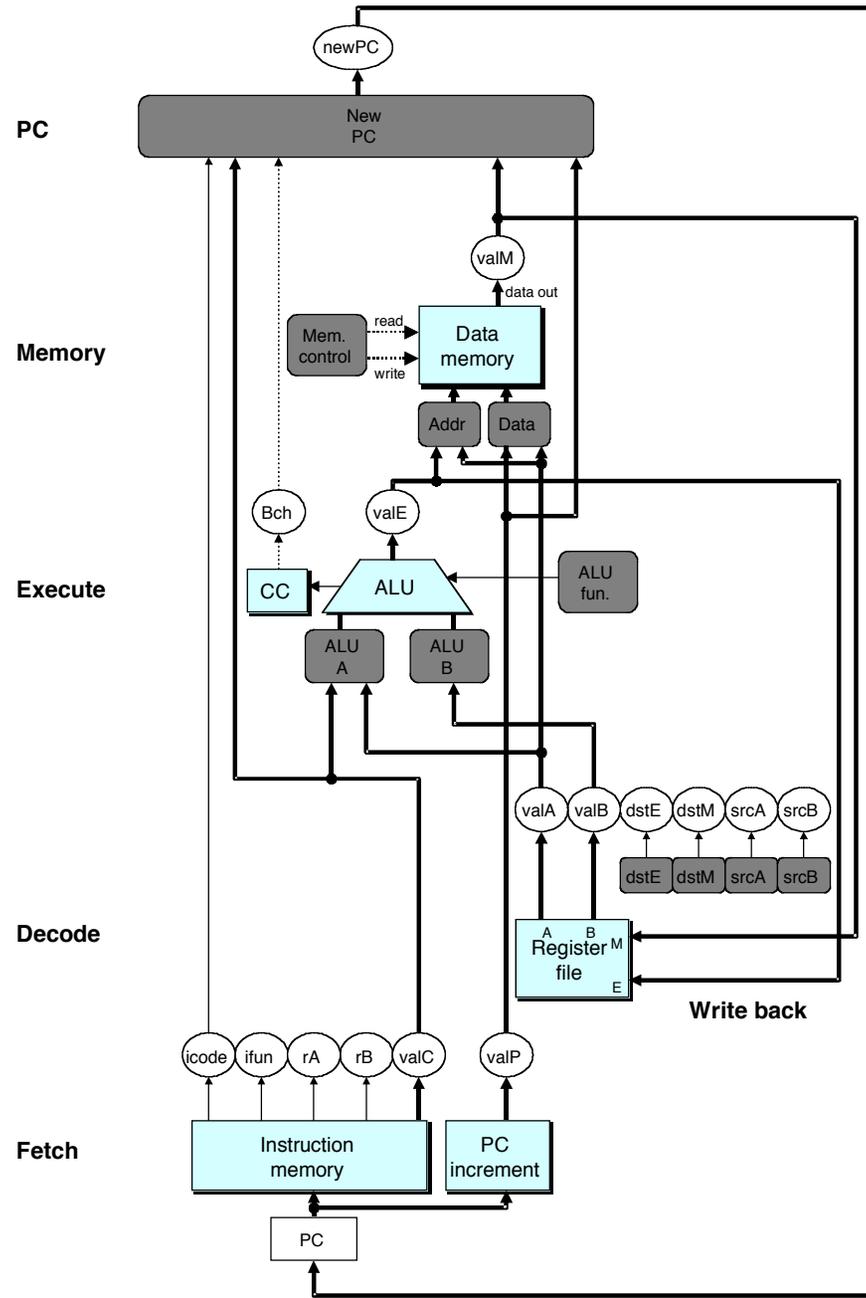
## Key

- **Blue boxes:**  
predesigned hardware blocks
  - E.g., memories, ALU
- **Gray boxes:**  
control logic
  - Describe in HCL
- **White ovals:**  
labels for signals
- **Thick lines:**  
32-bit word values
- **Thin lines:**  
4-8 bit values
- **Dotted lines:**  
1-bit values




# Fetch Logic

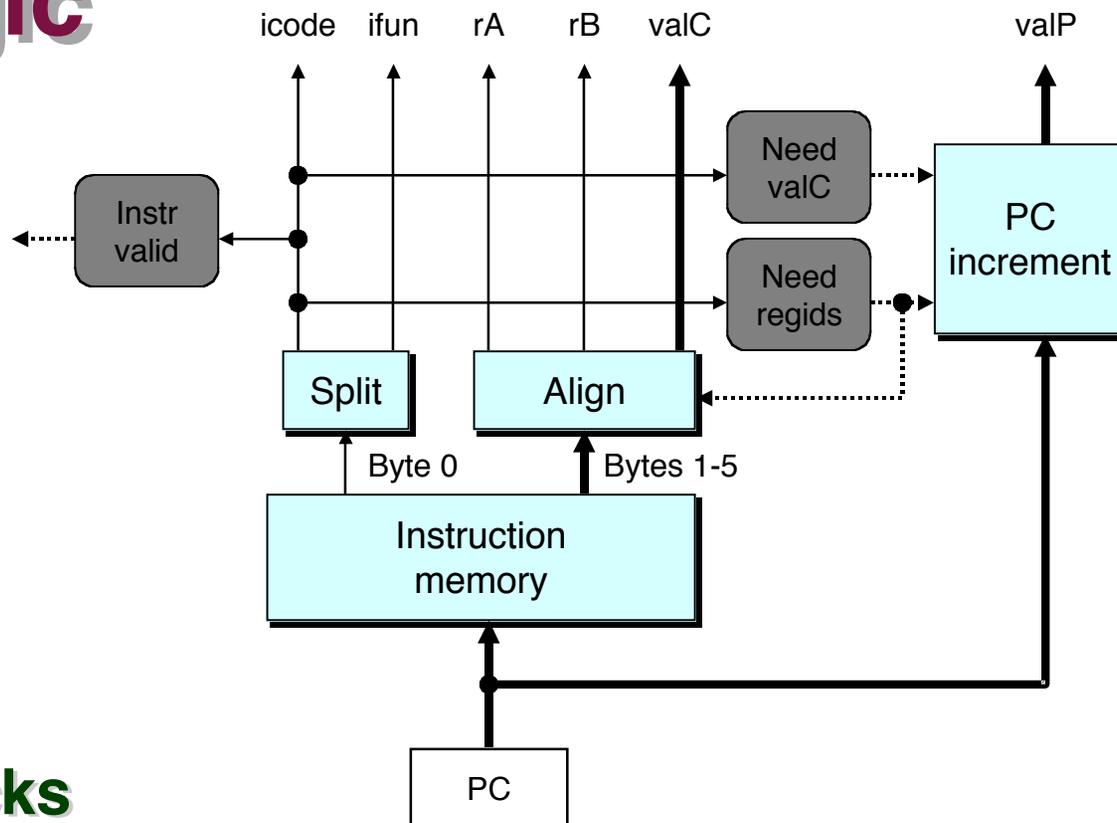

## Predefined Blocks

- PC: Register containing PC
- Instruction memory: Read 6 bytes (PC to PC+5)
- Split: Divide instruction byte into icode and ifun
- Align: Get fields for rA, rB, and valC


# Fetch Logic

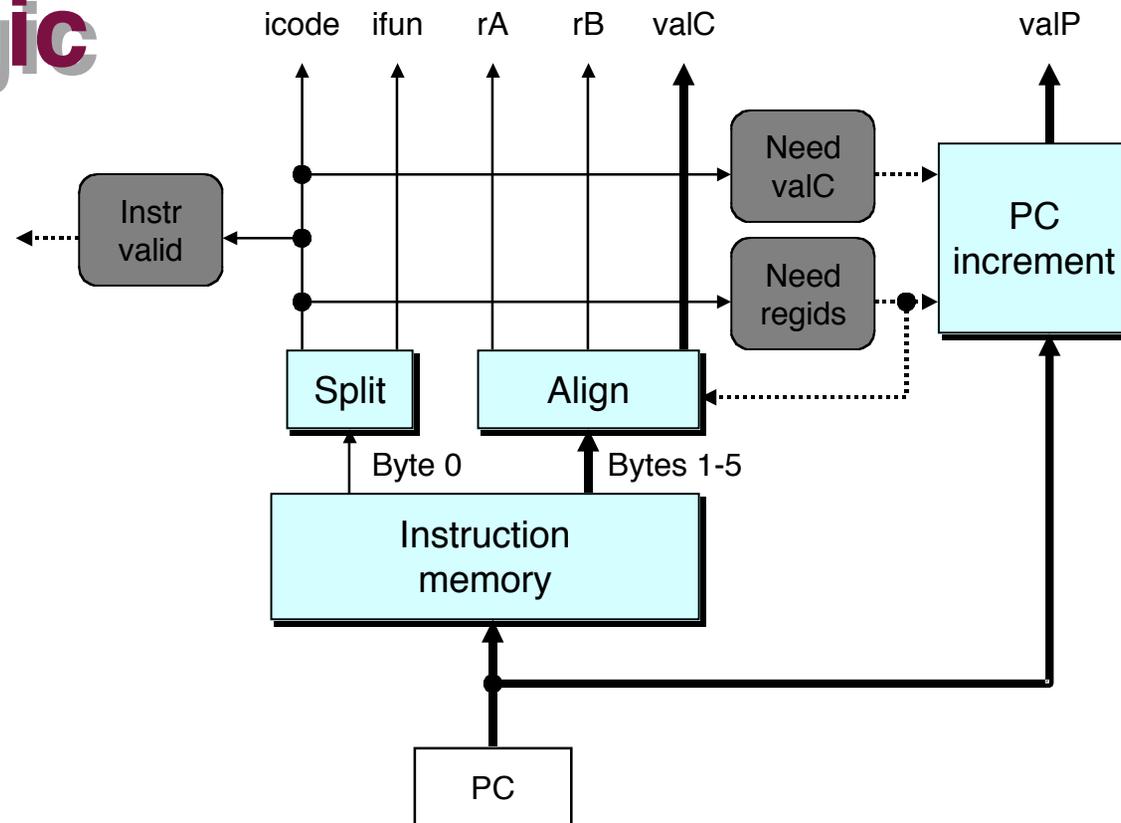

## Control Logic

- **Instr. Valid: Is this instruction valid?**
- **Need regids: Does this instruction have a register bytes?**
- **Need valC: Does this instruction have a constant word?**

# Fetch Control Logic

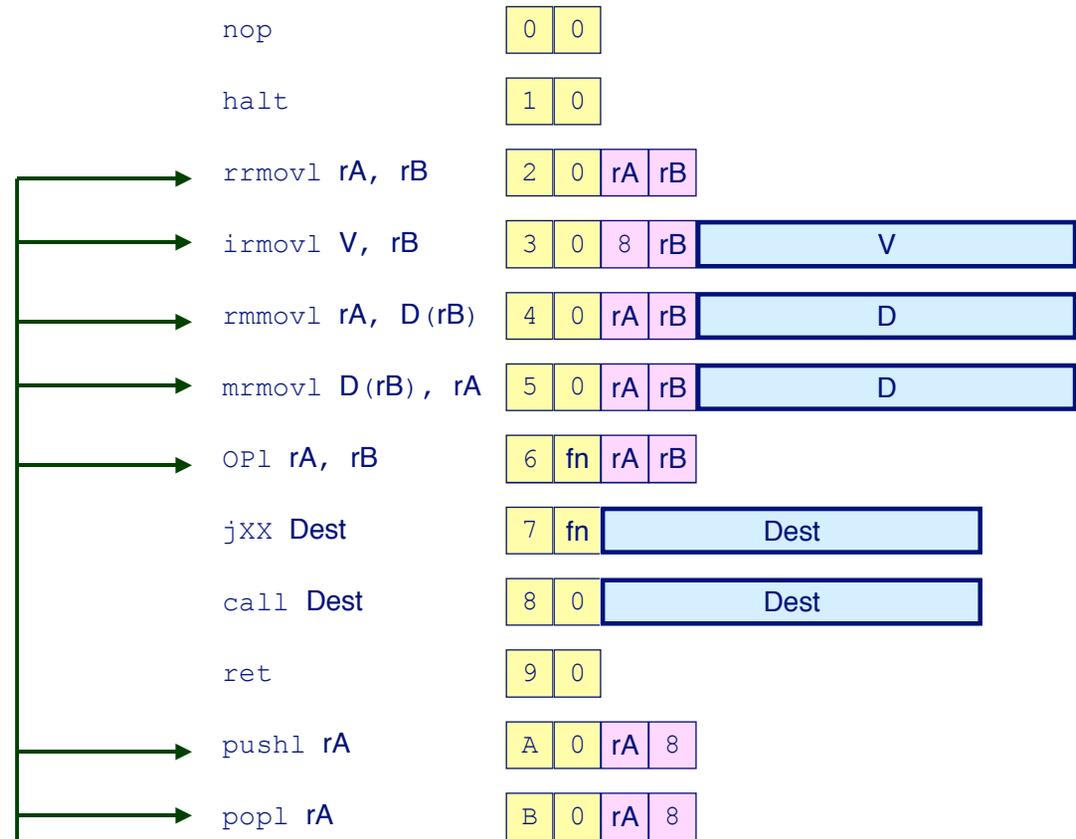

```
bool need_regids =
    icode in { IRRMOVL, IOPL, IPUSHL, IPOPL,
              IIRMOVL, IRMMOVL, IMRMOVL };
```

```
bool instr_valid = icode in
    { INOP, IHALT, IRRMOVL, IIRMOVL, IRMMOVL, IMRMOVL,
      IOPL, IJXX, ICALL, IRET, IPUSHL, IPOPL };
```


# Decode Logic

## Register File

- Read ports A, B
- Write ports E, M
- Addresses are register IDs or 8 (no access)
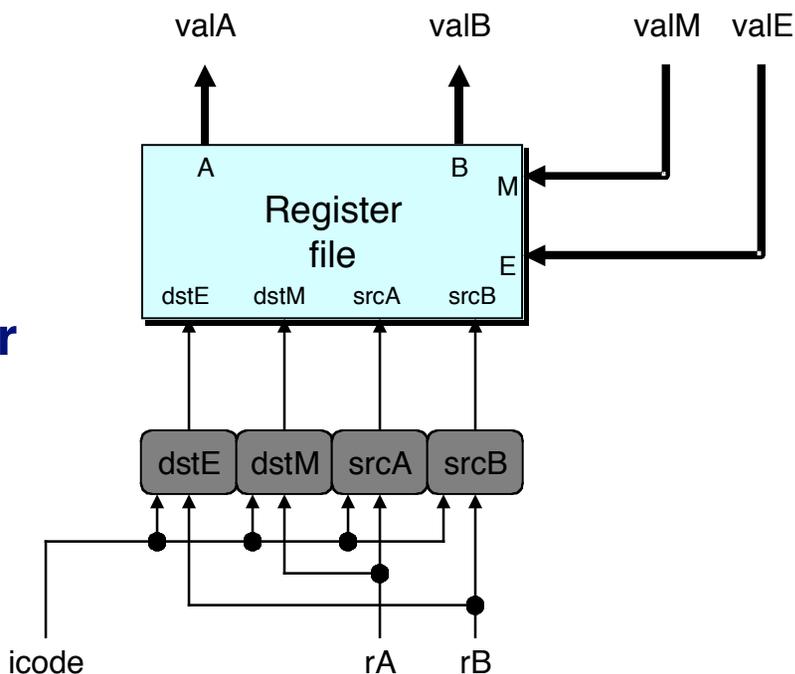
## Control Logic

- srcA, srcB: read port addresses
- dstA, dstB: write port addresses



# A Source

	OPl rA, rB	
Decode	valA ← R[rA]	Read operand A
	rmmovl rA, D(rB)	
Decode	valA ← R[rA]	Read operand A
	popl rA	
Decode	valA ← R[%esp]	Read stack pointer
	jXX Dest	
Decode		No operand
	call Dest	
Decode		No operand
	ret	
Decode	valA ← R[%esp]	Read stack pointer

```
int srcA = [
    icode in { IRRMOVL, IRMMOVL, IOPL, IPUSHL } : rA;
    icode in { IPOPL, IRET } : RESP;
    1 : RNONE; # Don't need register
```

```
];
```

# E Destination

	OPl rA, rB	
Write-back	R[rB] ← valE	Write back result
	rmmovl rA, D(rB)	
Write-back		None
	popl rA	
Write-back	R[%esp] ← valE	Update stack pointer
	jXX Dest	
Write-back		None
	call Dest	
Write-back	R[%esp] ← valE	Update stack pointer
	ret	
Write-back	R[%esp] ← valE	Update stack pointer

```
int dstE = [
    icode in { IRRMOVL, IIRMOVL, IOPL } : rB;
    icode in { IPUSHL, IPOPL, ICALL, IRET } : RESP;
    1 : RNONE; # Don't need register
```

```
];
```


# Execute Logic

## Units

- **ALU**
  - Implements 4 required functions
  - Generates condition code values
- **CC**
  - Register with 3 condition code bits
- **bcond**
  - Computes branch flag
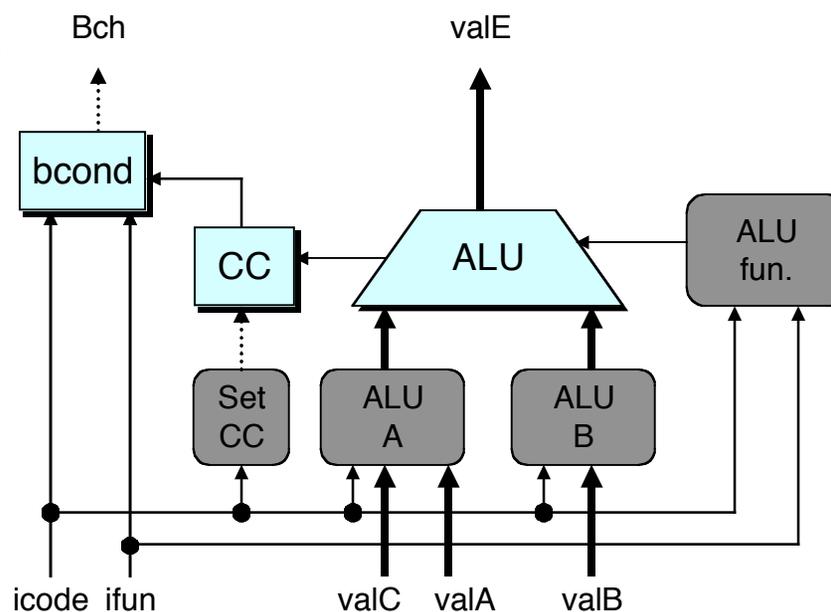
## Control Logic

- **Set CC:** Should condition code register be loaded?
- **ALU A:** Input A to ALU
- **ALU B:** Input B to ALU
- **ALU fun.:** What function should ALU compute?



# ALU A Input

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int aluA = [
    icode in { IRRMOVL, IOPL } : valA;
    icode in { IIRMOVL, IRMMOVL, IMRMOVL } : valC;
    icode in { ICALL, IPUSHL } : -4;
    icode in { IRET, IPOPL } : 4;
    # Other instructions don't need ALU
```

# ALU Operation

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int alufun = [  
    icode == IOPL : ifun;  
    1 : ALUADD;  
];
```


# Memory Logic

## Memory

- Reads or writes memory word
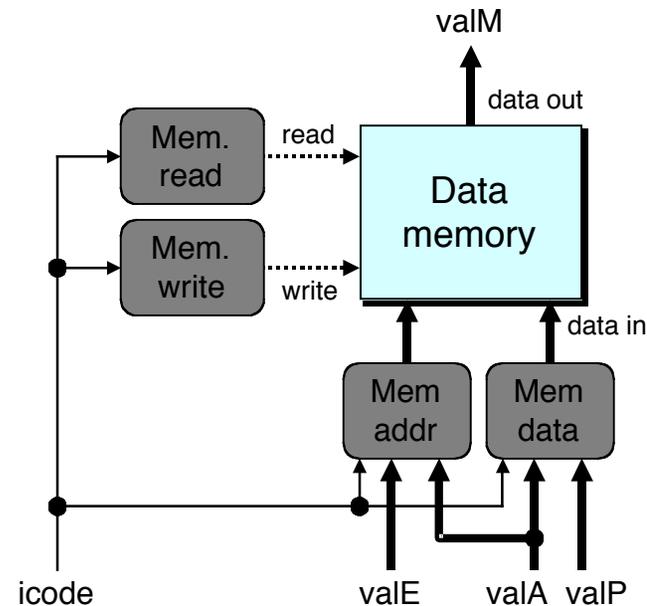
## Control Logic

- Mem. read: should word be read?
- Mem. write: should word be written?
- Mem. addr.: Select address
- Mem. data.: Select data



# Memory Address

	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
int mem_addr = [
    icode in { IRMMOVL, IPUSHL, ICALL, IMRMOVL } : valE;
    icode in { IPOPL, IRET } : valA;
    # Other instructions don't need address
```

# Memory Read


	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
bool mem_read = icode in { IMRMOVL, IPOPL, IRET };
```

# PC Update Logic

## New PC

- Select next value of PC

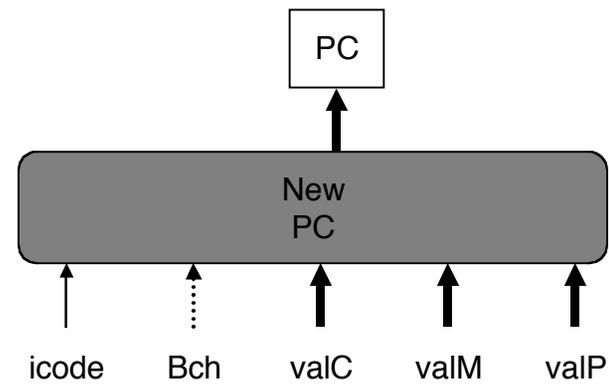


# PC Update

	OPl rA, rB	
PC update	PC ← valP	Update PC
	rmmovl rA, D(rB)	
PC update	PC ← valP	Update PC
	popl rA	
PC update	PC ← valP	Update PC
	jXX Dest	
PC update	PC ← Bch ? valC : valP	Update PC
	call Dest	
PC update	PC ← valC	Set PC to destination
	ret	
PC update	PC ← valM	Set PC to return address

```
int new_pc = [  
    icode == ICALL : valC;  
    icode == IJXX && Bch : valC;  
    icode == IRET : valM;  
    1 : valP;  
];
```

# SEQ Operation

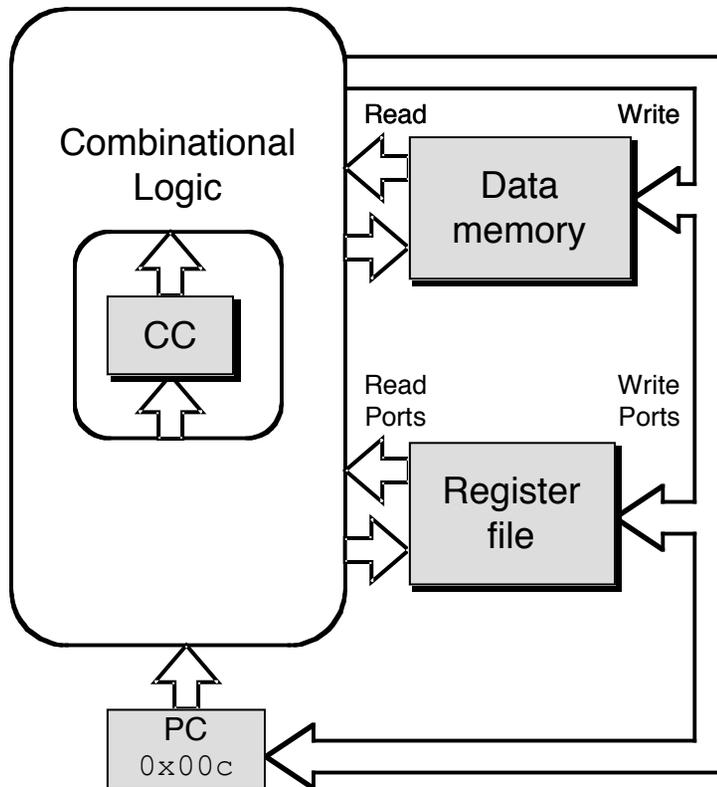

## State



- PC register
- Cond. Code register
- Data memory
- Register file

*All updated as clock rises*

## Combinational Logic



- ALU
- Control logic
- Memory reads
  - Instruction memory
  - Register file
  - Data memory

# SEQ Operation #2

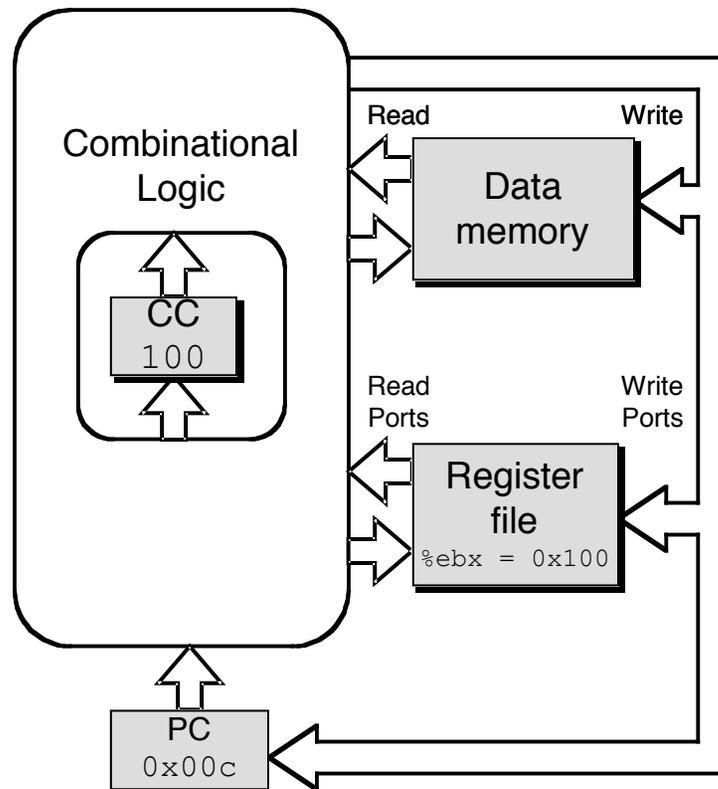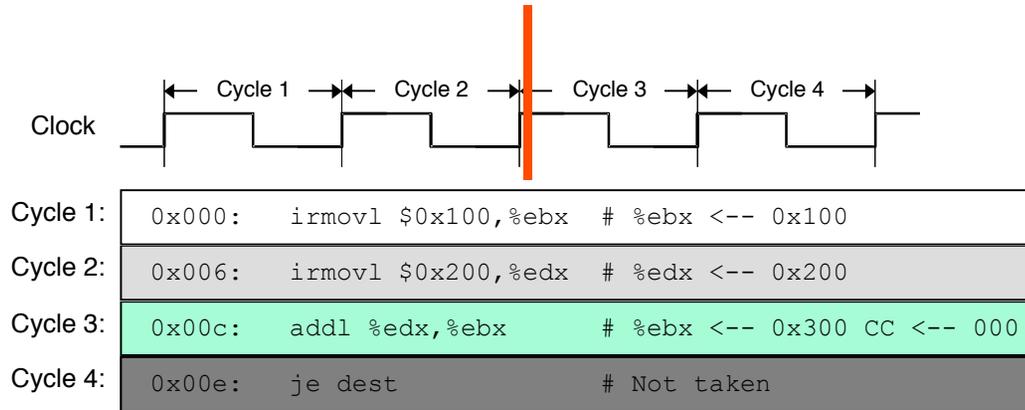



- state set according to second `irmovl` instruction
- combinational logic starting to react to state changes

# SEQ Operation #3

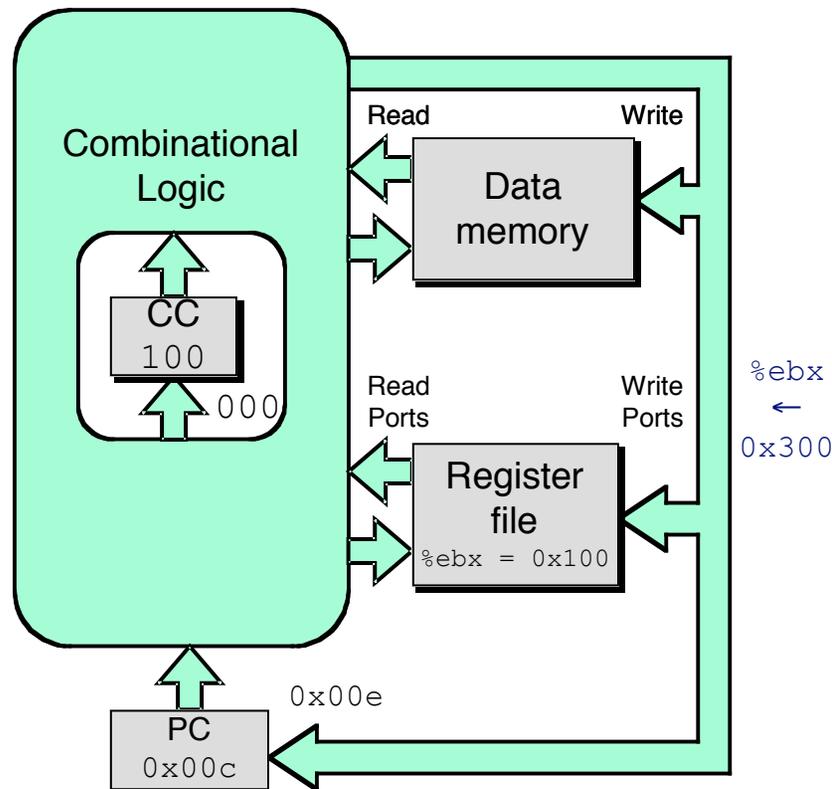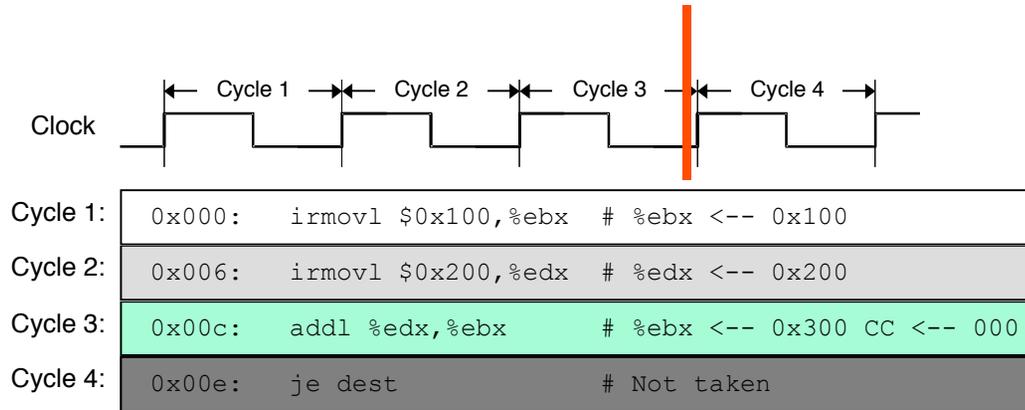



- state set according to second `irmovl` instruction
- combinational logic generates results for `addl` instruction

# SEQ Operation #4

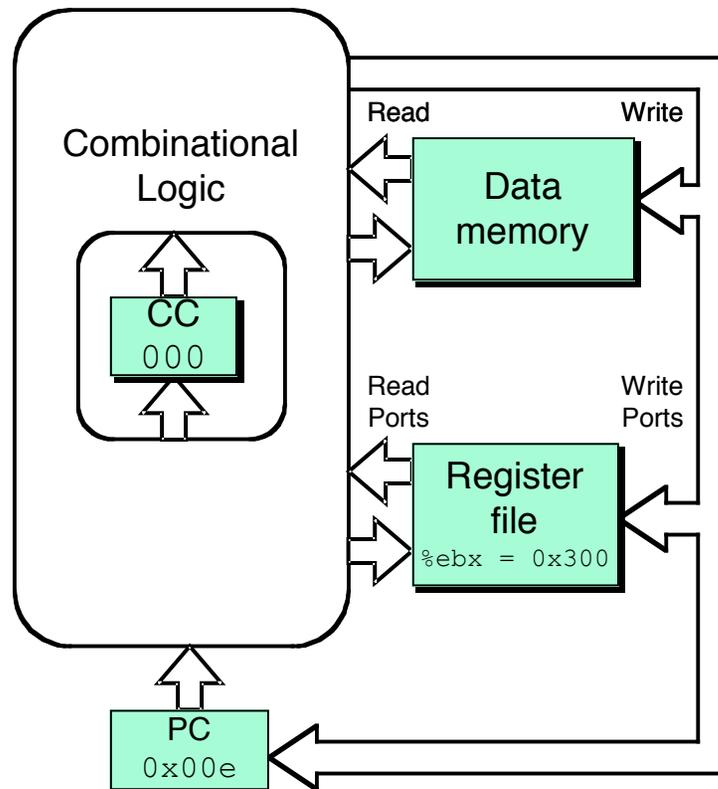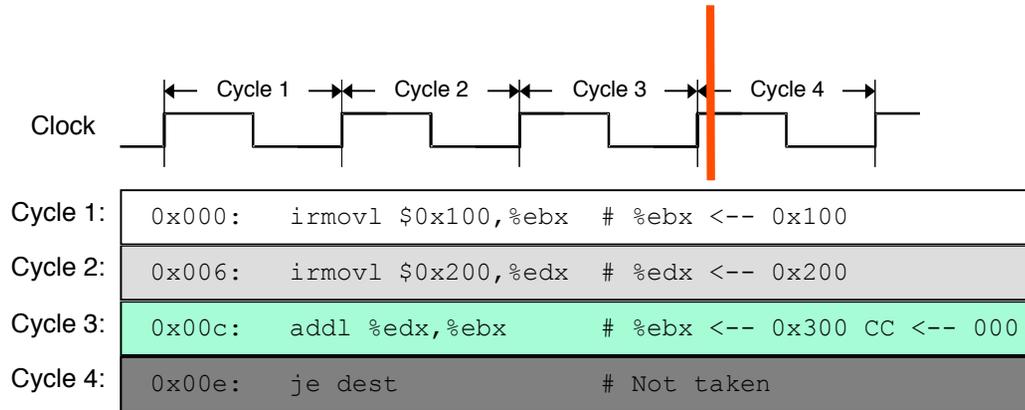

- **state set according to addl instruction**
- **combinational logic starting to react to state changes**

# SEQ Operation #5

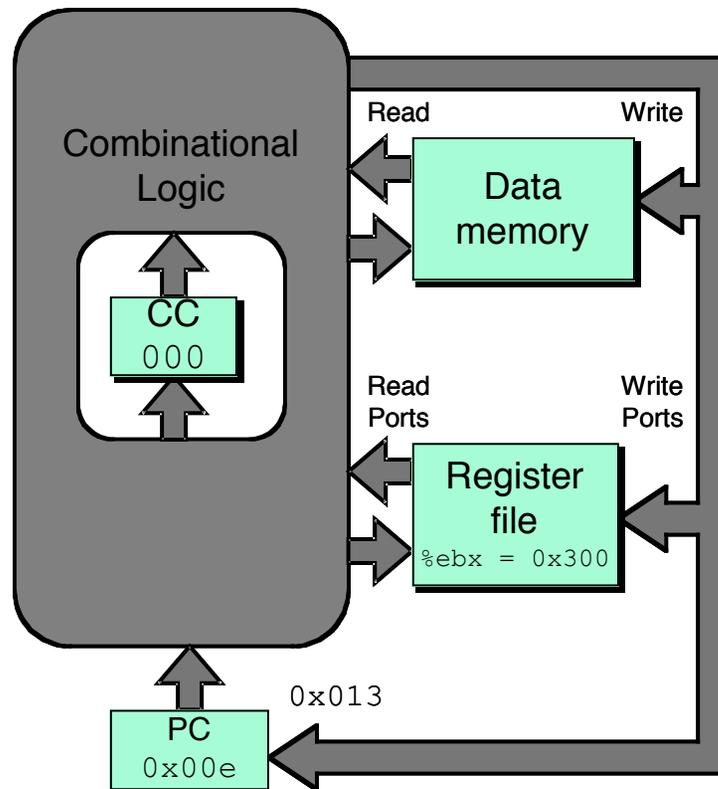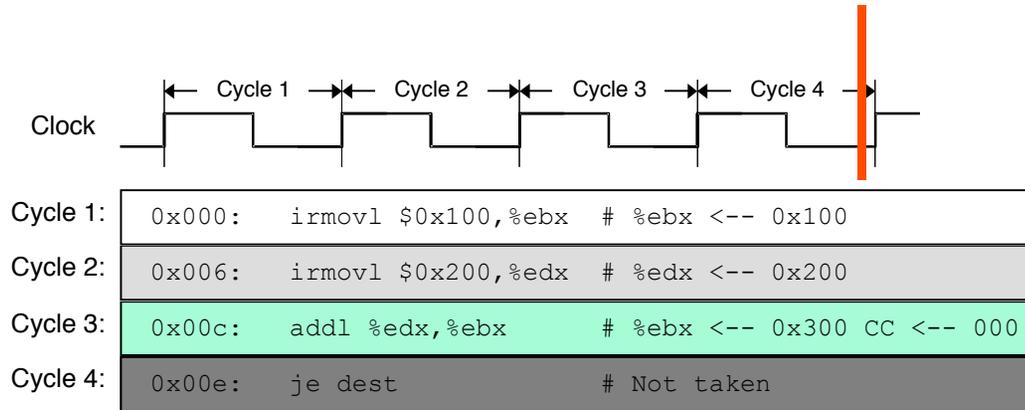

- **state set according to addl instruction**
- **combinational logic generates results for je instruction**

# SEQ Summary

## Implementation

- Express every instruction as series of simple steps
- Follow same general flow for each instruction type
- Assemble registers, memories, predesigned combinational blocks
- Connect with control logic

## Limitations

- Too slow to be practical
- In one cycle, must propagate through instruction memory, register file, ALU, and data memory
- Would need to run clock very slowly
- Hardware units only active for fraction of clock cycle